

APPLICATION NOTES

SP/SPW Series Trim Function

The following information is provided to allow quick calculation of the trim resistor value for a desired output voltage. The general procedure for calculating a trim resistor is as follows:


1. Determine the desired output voltage (V_o)
2. Select Equation. (Trim Low/Trim High)
3. Use the data in Table 1 to complete the equation.
4. Evaluate.

In order to trim low use Equation 1 and Table 1 to calculate resistor R_{TL} for the desired output voltage.

Equation 1: Trim Low

$$R_{TL} = \left[\frac{V_o - V_{REF}}{\left(\frac{V_{REF}}{R_L}\right) - \left(\frac{V_o - V_{REF}}{R_H}\right)} \right] - R_{LIM}$$

V_o - Desired output voltage.
All resistor values in K ohms.

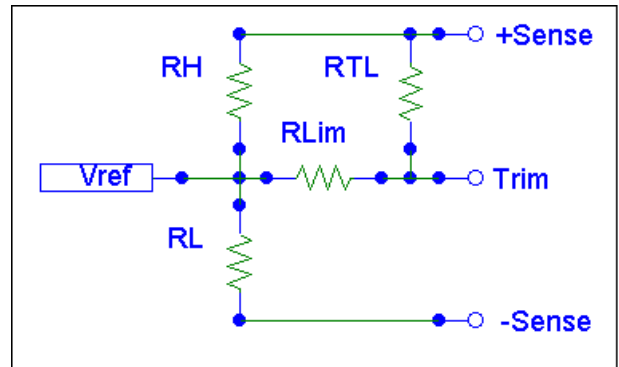


Schematic 1: Trim Low

In order to trim high use Equation 2 and Table 1 to calculate resistor R_{TH} for the desired output voltage.

Equation 2: Trim High

$$R_{TH} = \left[\frac{V_{REF}}{\left(\frac{V_o - V_{REF}}{R_H}\right) - \left(\frac{V_{REF}}{R_L}\right)} \right] - R_{LIM}$$

V_o - Desired output voltage.
All resistor values in K ohms.

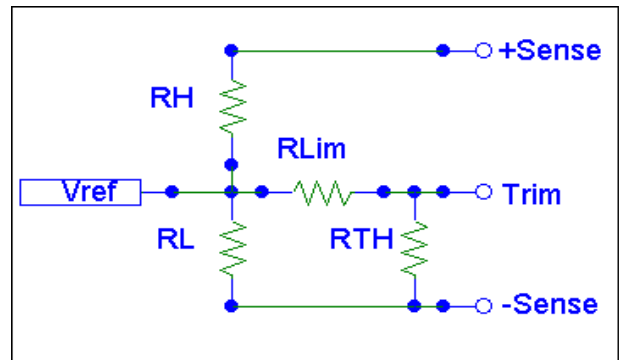

Schematic 2: Trim High

MODEL (Output Voltage)	R_H (K OHMS)	R_{LIM} (K OHMS)	R_L (K OHMS)	V_{REF} (VOLTS)
3.3V	0.750	0.499	2.32	2.495
5.0V	2.49	10.0	2.49	2.495
8.0V	5.49	10.0	2.49	2.495
9.0V	6.49	10.0	2.49	2.495
12.0V	9.53	13.7	2.49	2.495
15.0V	12.4	13.7	2.49	2.495
24.0V	21.5	15.4	2.49	2.495
26.0V	17.6	15.4	1.87	2.495
32.0V	23.7	12.7	2.00	2.495

Table 1 : Trim Low/High Data Table.

Note: Output trim +/- 10% max.